


## Assignment #2, Total: 10 pts

Name:


NetID:

### Chapter 4. Diodes

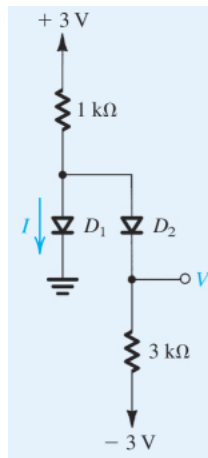1. (0.5 pts) Assuming that the diodes in the circuits are *ideal*, find the values of the labeled voltage and current.




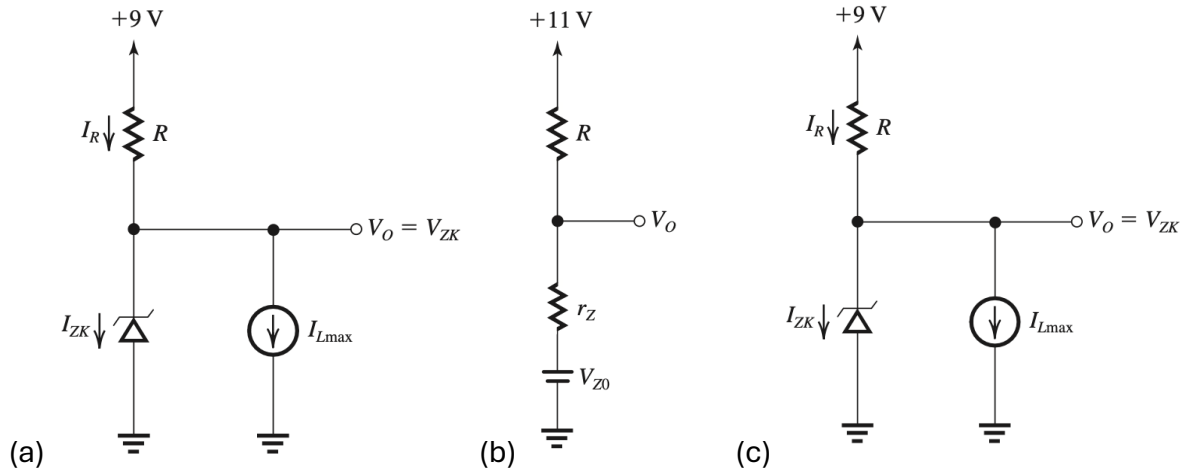2. (2 pts) Design a zener regulator circuit using a 7.5-V zener specified at 10 mA. The zener has an incremental resistance  $r_z = 30\ \Omega$  and a knee current of 0.5 mA. The regulator operates from a 10-V supply and delivers a nominal current of 5 mA to the load.
- (a) What is the value of  $R$  you have chosen?
- (b) What is the output voltage when both the supply is 10% high and the load is removed?
- (c) What is the largest load current that can be delivered while the zener operates at a current no lower than the knee current while the supply is 10% low?



### Chapter 5. MOS Field-Effect Transistors (MOSFETs)

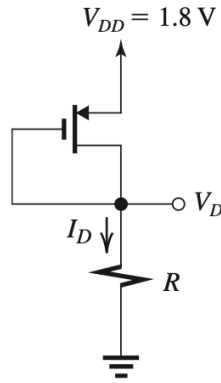
3. (1 pt) The PMOS transistor in the circuit has  $V_t = -0.5$  V,  $\mu_p C_{ox} = 100$   $\mu\text{A}/\text{V}^2$ ,  $L = 0.18$   $\mu\text{m}$ , and  $\lambda = 0$ . Find the values required for  $W$  and  $R$  in order to establish a drain current of 160  $\mu\text{A}$  and a voltage  $V_D$  of 0.8 V.



4. (1 pt) For a particular MOSFET operating in the saturation region at a constant  $v_{GS}$ ,  $i_D$  is found to be 200  $\mu\text{A}$  for  $v_{DS} = 1$  V and 205  $\mu\text{A}$  for  $v_{DS} = 1.5$  V. Find the values of  $r_o$ ,  $V_A$ , and  $\lambda$ .


## Chapter 6. Bipolar Junction Transistors (BJTs)

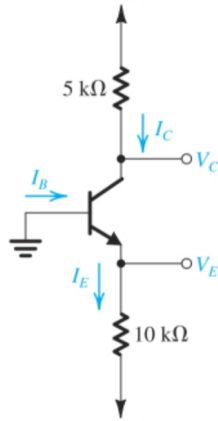5. (1 pt) In the circuit shown in the figure, the power supplies are  $\pm 3\text{ V}$  and the voltage at the emitter was measured and found to be  $-0.7\text{ V}$ . If  $\beta = 50$ , find  $I_E$ ,  $I_B$ ,  $I_C$ , and  $V_C$ .



## Chapter 7. Transistor Amplifiers

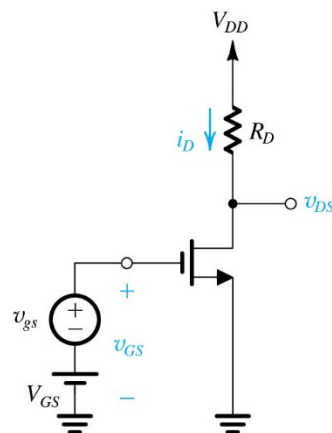6. (1 pt) A designer wants to create a BJT amplifier with a  $g_m$  of 20 mA/V and a base input resistance of 4000  $\Omega$  or more. What collector-bias current should she choose? What is the minimum  $\beta$  she can tolerate for the transistor used?
7. (1.5 pt) Consider the amplifier of the following circuit:  $V_{DD} = 5$  V,  $R_D = 24$  k $\Omega$ ,  $(W/L) = 1$  mA/V<sup>2</sup>, and  $V_t = 1$  V.
- (a) Find the coordinates of the two end points of the saturation-region segment of the amplifier transfer characteristic, that is, points A and B.
- (b) If the amplifier is biased to operate with an overdrive voltage  $V_{OV}$  of 0.5 V, find the coordinates of the bias point Q on the transfer characteristic. Also, find the value of  $I_D$  and of the incremental gain  $A_v$  at the bias point.



8. (2 pts) The following figure shows a discrete-circuit amplifier. The input signal  $v_{\text{sig}}$  is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage signal that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite). All capacitors behave as short circuits for signals and as open circuits for dc.
- (a) If the transistor has  $V_t = 1 \text{ V}$ , and  $k_n = 4 \text{ mA/V}^2$ , verify that the bias circuit establishes  $V_{GS} = 1.5 \text{ V}$ ,  $I_D = 0.5 \text{ mA}$ , and  $V_D = +7.0 \text{ V}$ . That is, assume these values, and verify that they are consistent with the values of the circuit components and the device parameters.
- (b) Find  $g_m$  and  $r_o$  if  $V_A = 100 \text{ V}$ .
- (c) Find  $R_{\text{in}}$ ,  $v_{gs}/v_{\text{sig}}$ ,  $v_o/v_{gs}$ , and  $v_o/v_{\text{sig}}$ .

