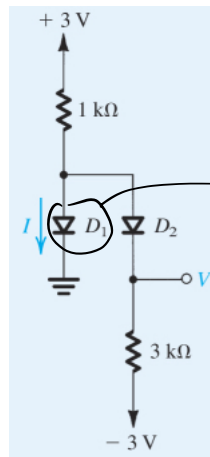


Assignment #2, Total: 10 pts

Name: Aditya Rajesh NetID: arr210

Chapter 4. Diodes

1. (0.5 pts) Assuming that the diodes in the circuits are **ideal**, find the values of the labeled voltage and current.



Since $D1$ is ON and ideal, it acts like a short circuit.

Therefore, the voltage at the node where $D1$ connects is $0V$, because it is directly connected to ground through $D1$.

$$V = IR$$


$$3 - 0 = I(1k)$$

$$I = \frac{3}{1k}$$

$$I = 0.003 A$$

$$= 3 mA$$

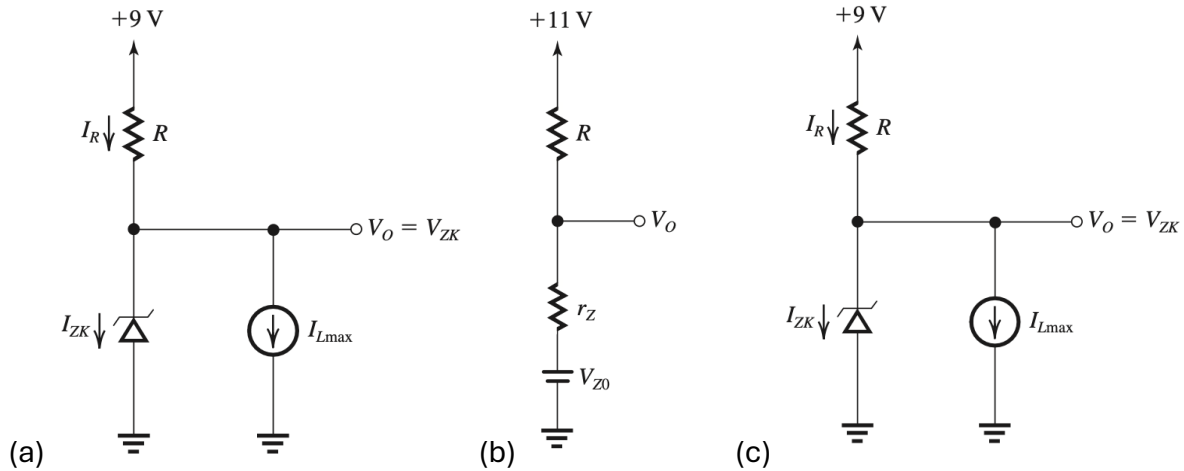2. (2 pts) Design a zener regulator circuit using a 7.5-V zener specified at 10 mA. The zener has an incremental resistance $r_z = 30 \Omega$ and a knee current of 0.5 mA. The regulator operates from a 10-V supply and delivers a nominal current of 5 mA to the load.
- (a) What is the value of R you have chosen?
- (b) What is the output voltage when both the supply is 10% high and the load is removed?
- (c) What is the largest load current that can be delivered while the zener operates at a current no lower than the knee current while the supply is 10% low?



a.

$$I_R = I_Z + I_L$$

$$= 10\text{ mA} + 5\text{ mA}$$

$$= 15\text{ mA}$$

$$R = \frac{V_s - V_Z}{I_R}$$

$$= \frac{10 - 7.5}{15 \times 10^{-3}}$$

$$= \frac{2.5}{0.015}$$

$$= 166.67 \Omega$$

b. $V_s = 1.1 \times 10 = 11\text{ V}$

$$I_Z = \frac{V_s - V_Z}{R}$$

$$= \frac{11 - 7.5}{166.67}$$

$$= \frac{3.5}{166.67}$$

$$= 21\text{ mA}$$

$$V_o = V_Z + (I_Z) \cdot r_z$$

$$= 7.5 + (21 \cdot 10^{-3}) \cdot 30$$

$$= 7.5 + 0.63$$

$$= 8.13\text{ V}$$

c. $V_s = 0.9 \cdot 10$

$$= 9\text{ V}$$

$$I_R = \frac{V_s - V_Z}{R}$$

$$= \frac{9 - 7.5}{166.67}$$

$$= \frac{1.5}{166.67}$$

$$= 9\text{ mA}$$

$$I_{Zk} = 0.5\text{ mA}$$

$$I_{Lmax} = I_R - I_{Zk}$$

$$= 9\text{ mA} - 0.5\text{ mA}$$

$$= 8.5\text{ mA}$$

Chapter 5. MOS Field-Effect Transistors (MOSFETs)

3. (1 pt) The PMOS transistor in the circuit has $V_t = -0.5 \text{ V}$, $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$, $L = 0.18 \mu\text{m}$, and $\lambda = 0$. Find the values required for W and R in order to establish a drain current of $160 \mu\text{A}$ and a voltage V_D of 0.8 V .

$$V_t = -0.5 \text{ V}$$

$$\mu_p C_{ox} = 100 \frac{\mu\text{A}}{\text{V}^2}$$

$$L = 0.18 \mu\text{m}$$

$$V_{DD} = 1.8 \text{ V}$$

$$V_D = 0.8 \text{ V}$$

$$I_D = 160 \mu\text{A}$$

$$V_{sg} = V_{DD} - V_D$$

$$V_{sg} = 1.8 \text{ V} - 0.8 \text{ V} = 1.0 \text{ V}$$

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{sg} - |V_t|)^2$$


$$W = \frac{2 I_D L}{\mu_p C_{ox} (V_{sg} - |V_t|)^2}$$

$$W = \frac{2 \cdot (160 \cdot 10^{-6}) \cdot (0.18 \cdot 10^{-6})}{(100 \cdot 10^{-6}) \cdot (1.0 - 0.5)^2}$$

$$W = \frac{57.6 \cdot 10^{-12}}{25 \cdot 10^{-6}}$$

$$= 2.304 \cdot 10^{-6} \text{ m}$$

$$= 2.304 \mu\text{m}$$

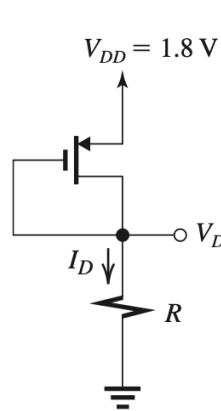

$$R = \frac{V_D}{I_D}$$

$$R = \frac{0.8 \text{ V}}{160 \cdot 10^{-6} \text{ A}}$$

$$R = 5000 \Omega$$

4. (1 pt) For a particular MOSFET operating in the saturation region at a constant v_{GS} , i_D is found to be $200 \mu\text{A}$ for $v_{DS} = 1 \text{ V}$ and $205 \mu\text{A}$ for $v_{DS} = 1.5 \text{ V}$. Find the values of r_o , V_A , and λ .

$$i_{D1} = 200 \cdot 10^{-6}$$

$$i_{D2} = 205 \cdot 10^{-6}$$

$$V_{DS1} = 1.0 \text{ V}$$

$$V_{DS2} = 1.5 \text{ V}$$

$$\Delta V_{DS} = V_{DS2} - V_{DS1} \\ = 1.5 - 1.0 \\ = 0.5 \text{ V}$$

$$\Delta i_D = i_{D2} - i_{D1} \\ = (205 - 200) \cdot 10^{-6} \\ = 5 \cdot 10^{-6} \text{ A}$$

$$r_o = \frac{\Delta V_{DS}}{\Delta i_D}$$

$$r_o = \frac{0.5 \text{ V}}{5 \cdot 10^{-6}}$$

$$= 100000 \Omega$$

$$\lambda = \frac{1}{r_o \times i_{D1}}$$

$$\lambda = \frac{1}{100000 \cdot (200 \cdot 10^{-6})}$$

$$\lambda = \frac{1}{20} \\ = 0.05 \text{ V}^{-1}$$

$$V_A = \frac{1}{\lambda}$$

$$V_A = \frac{1}{0.05}$$

$$= 20 \text{ V}$$

Chapter 6. Bipolar Junction Transistors (BJTs)

5. (1 pt) In the circuit shown in the figure, the power supplies are $\pm 3\text{ V}$ and the voltage at the emitter was measured and found to be -0.7 V . If $\beta = 50$, find I_E , I_B , I_C , and V_C .


$$V_E = -0.7\text{ V}$$

Power Supplies: $\pm 3\text{ V}$

$$\beta = 50$$

$$R_E = 10\text{ k}\Omega$$

$$R_C = 5\text{ k}\Omega$$

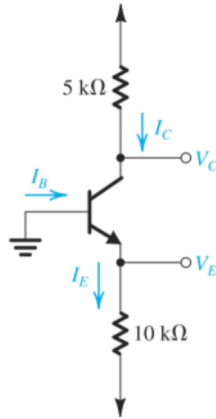

$$I_E = \frac{V_E - V_-}{R_E}$$

$$I_E = \frac{-0.7 - (-3)}{10000}$$

$$I_E = \frac{2.3}{10000}$$

$$I_E = 0.00023\text{ A}$$

$$I_E = 0.230\text{ mA}$$

$$I_C = \frac{\beta}{\beta + 1} I_E$$

$$I_C = \frac{50}{51} \cdot 0.00023$$

$$I_C = 0.00022549\text{ A}$$

$$I_C = 0.225\text{ mA}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_B = \frac{0.00022549}{50}$$

$$I_B = 4.5098 \cdot 10^{-6}\text{ A}$$

$$I_B = 4.510\text{ }\mu\text{A}$$

$$V_C = V_+ - (I_C \cdot R_C)$$

$$V_C = 3 - (0.00022549 \cdot 5000)$$

$$V_C = 3 - 1.12745$$

$$V_C = 1.8725\text{ V}$$

$$V_C = 1.873\text{ V}$$

Chapter 7. Transistor Amplifiers

6. (1 pt) A designer wants to create a BJT amplifier with a g_m of 20 mA/V and a base input resistance of 4000 Ω or more. What collector-bias current should she choose? What is the minimum β she can tolerate for the transistor used?

$$g_m = \frac{I_C}{V_T}$$

$$I_C = g_m \cdot V_T$$

$$I_C = (20 \cdot 10^{-3}) \cdot (25 \cdot 10^{-3})$$

$$I_C = 0.5 \cdot 10^{-3}$$

$$I_C = 0.5 \text{ mA}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

$$\beta = r_{\pi} \cdot g_m$$

$$\beta = 4000 \cdot (20 \cdot 10^{-3})$$

$$\beta = 4000 \cdot 0.02$$

$$\beta = 80$$

7. (1.5 pt) Consider the amplifier of the following circuit: $V_{DD} = 5 \text{ V}$, $R_D = 24 \text{ k}\Omega$, $(W/L) = 1 \text{ mA/V}^2$, and $V_t = 1 \text{ V}$.

(a) Find the coordinates of the two end points of the saturation-region segment of the amplifier transfer characteristic, that is, points A and B.

(b) If the amplifier is biased to operate with an overdrive voltage V_{OV} of 0.5 V, find the coordinates of the bias point Q on the transfer characteristic. Also, find the value of I_D and of the incremental gain A_v at the bias point.

a. $V_{GS} = V_t = 1 \text{ V}$
 $I_D = 0$

$$V_{DS} = V_{DD} - I_D R_D$$

$$= 5 - 0$$

$$= 5$$

Point A: $(V_{GS}, V_{DS}) = (1 \text{ V}, 5 \text{ V})$

$$V_{DS} = V_{GS} - V_t$$

$$V_{DS} = V_{DD} - I_D R_D \quad \text{and} \quad I_D = \frac{1}{2} k' \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$V_{DD} - \left(\frac{1}{2} k' \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 \right) R_D = V_{GS} - V_t$$

$$5 - \left(\frac{1}{2} (1 \cdot 10^{-3}) (1) (V_{GS} - 1)^2 \right) (24 \cdot 10^3) = V_{GS} - 1$$

$$5 - (12) (V_{GS} - 1)^2 = V_{GS} - 1$$

$$-12 V_{GS}^2 + 24 V_{GS} - 7 = V_{GS} - 1$$

$$-12 V_{GS}^2 + 23 V_{GS} - 6 = 0$$

$$V_{GS} = 0.311 \text{ V}$$

$$I_D = \frac{1}{2} (1 \cdot 10^{-3}) (0.311 - 1)^2$$

$$I_D = \frac{1}{2} (1 \cdot 10^{-3}) (-0.689)^2$$

$$I_D = 0.5 \cdot 1 \cdot 10^{-3} \cdot 0.474$$

$$I_D = 0.237 \text{ mA}$$

Point B: $(V_{GS}, V_{DS}) = (0.311 \text{ V}, -0.689 \text{ V})$

$$V_{DS} = 5 - (0.237 \cdot 10^{-3}) (24 \cdot 10^3)$$

$$V_{DS} = 5 - 5.688$$

$$V_{DS} = -0.688 \text{ V}$$

b. $V_{OV} = 0.5 \text{ V}$

$$V_{GS} = V_t + V_{OV}$$

$$= 1 + 0.5$$

$$= 1.5$$

$$I_D = \frac{1}{2} (1 \cdot 10^{-3}) (1) (0.5)^2$$

$$I_D = 0.5 \cdot 1 \cdot 10^{-3} \cdot 0.25$$

$$I_D = 0.125 \text{ mA}$$

$$V_{DS} = 5 - (0.125 \cdot 10^{-3}) (24 \cdot 10^3)$$

$$V_{DS} = 5 - 3$$

$$V_{DS} = 2 \text{ V}$$

Bias Point Q:

$$(V_{GS}, V_{DS}) = (1.5 \text{ V}, 2.0 \text{ V})$$

$$g_m = k' \left(\frac{W}{L} \right) V_{OV}$$

$$g_m = (1 \cdot 10^{-3}) (1) (0.5)$$


$$= 0.5 \frac{\text{mA}}{\text{V}}$$

$$A_v = -g_m R_D$$

$$A_v = -(0.5 \cdot 10^{-3}) (24 \cdot 10^3)$$

$$A_v = -12$$

$$A_v = -12$$

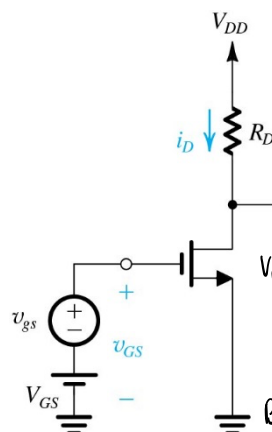


8. (2 pts) The following figure shows a discrete-circuit amplifier. The input signal v_{sig} is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage signal that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite). All capacitors behave as short circuits for signals and as open circuits for dc.

(a) If the transistor has $V_t = 1$ V, and $k_n = 4$ mA/V², verify that the bias circuit establishes $V_{GS} = 1.5$ V, $I_D = 0.5$ mA, and $V_D = +7.0$ V. That is, assume these values, and verify that they are consistent with the values of the circuit components and the device parameters.

(b) Find g_m and r_o if $V_A = 100$ V.

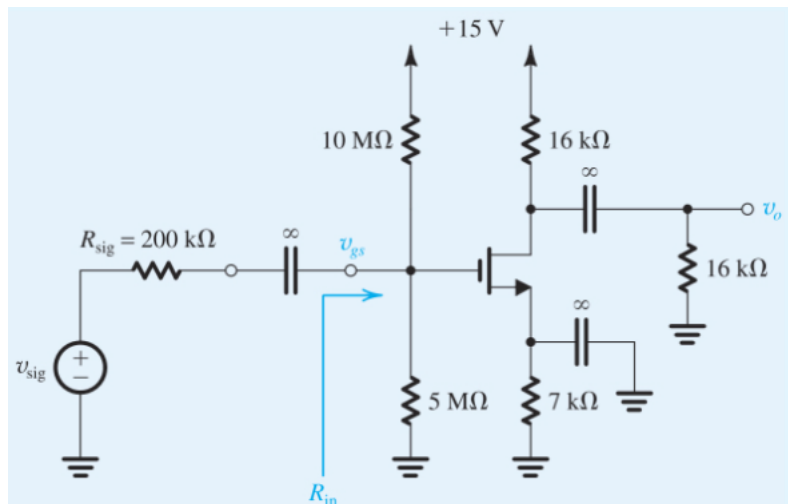(c) Find R_{in} , v_{gs}/v_{sig} , v_o/v_{gs} , and v_o/v_{sig} .



a.

$$V_t = 1 \text{ V}$$

$$k_n = 4 \frac{\text{mA}}{\text{V}^2}$$

$$= 0.004 \frac{\text{A}}{\text{V}^2}$$

$$V_{GS} = 1.5 \text{ V}$$

$$I_D = 0.5 \text{ mA}$$

$$V_D = 7.0 \text{ V}$$

$$I_D = \frac{k_n}{2} (V_{GS} - V_t)^2$$

$$I_D = \frac{0.004}{2} (1.5 - 1)^2$$

$$= 0.002 (0.5)^2$$

$$= 0.002 (0.25)$$

$$= 0.0005 \text{ A}$$

$$= 0.5 \text{ mA}$$

$$R_S = \left(\frac{1}{5 \text{ M}\Omega} + \frac{1}{7 \text{ k}\Omega} \right)^{-1}$$

$$R_S = \left(\frac{1}{5 \cdot 10^6} + \frac{1}{7 \cdot 10^3} \right)^{-1}$$

$$= (2 \cdot 10^{-7} + 1.4286 \cdot 10^{-4})^{-1}$$

$$= (1.4306 \cdot 10^{-4})^{-1}$$

$$= 6990 \Omega$$

$$r_o = \frac{V_A}{I_D}$$

$$= \frac{100}{0.5 \cdot 10^{-3}}$$

$$= 200 \cdot 10^3$$

$$= 200 \text{ k}\Omega$$

$$V_S = I_D \cdot R_S$$

$$= (0.5 \cdot 10^{-3}) \cdot 6990$$

$$= 3.495 \text{ V}$$

$$V_D = 15 \text{ V} - I_D R_D$$

$$= 15 - (0.5 \cdot 10^{-3}) (16 \cdot 10^3)$$

$$= 15 - 8$$

$$= 7.0 \text{ V}$$

b.

$$g_m = \frac{2 I_D}{V_{GS} - V_t}$$

$$g_m = \frac{2 \cdot 0.5 \cdot 10^{-3}}{1.5 - 1}$$

$$= \frac{10^{-3}}{0.5}$$

$$= 2 \cdot 10^{-3} \frac{\text{A}}{\text{V}}$$

$$= 2.0 \text{ mA/V}$$

c.

$$R_{in} = R_{G1} \parallel R_{G2} = \left(\frac{1}{10 \text{ M}\Omega} + \frac{1}{200 \text{ k}\Omega} \right)^{-1}$$

$$R_{in} = 196.08 \text{ k}\Omega$$

$$\frac{v_{gs}}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}}$$

$$\frac{v_{gs}}{v_{sig}} = \frac{196.08}{196.08 + 200}$$

$$= \frac{196.08}{396.08}$$

$$\frac{v_{gs}}{v_{sig}} = 0.495$$

$$\frac{v_o}{v_{gs}} = -g_m (R_D \parallel R_L \parallel r_o)$$

$$R_D \parallel R_L \parallel r_o = \left(\frac{1}{16 \text{ k}\Omega} + \frac{1}{16 \text{ k}\Omega} + \frac{1}{200 \text{ k}\Omega} \right)^{-1}$$

$$= 7692 \Omega$$

$$\frac{v_o}{v_{gs}} = -2 \cdot 10^{-3} \cdot 7692$$

$$= -15.384$$

$$\frac{v_o}{v_{sig}} = \left(\frac{v_o}{v_{gs}} \right) \left(\frac{v_{gs}}{v_{sig}} \right)$$

$$= (-15.385) (0.495)$$

$$= -7.616$$